

*“Heaven’s Light is Our Guide”*



# **Rajshahi University of Engineering & Technology**

## **Department of Computer Science & Engineering**

### **Lab Report**

**Course Code: CSE 3108**

**Experiment No:1**

| <b>Submitted By:</b>  | <b>Submitted To:</b>   |
|---|--|
| <b>Name: Farzana Haider</b><br><b>Roll: 2003026</b><br><b>Section: A</b><br><b>Year:3rd year Odd Semester</b> | <b>Name: Utsha Das</b><br><b>Lecturer</b><br><b>Department of CSE</b><br><b>RUET</b> |

**Name of the experiment:** Simulation of 2 to 4 decoder using Logisim Evolution software.

**Theory:**


A decoder is a combinational logic circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  output lines. In this experiment, we focus on a 2 to 4 decoder, which takes two inputs and generates four outputs. The inputs represent a binary number, and the outputs indicate which one of the four output lines is active based on the input combination.

**Experiment :**

Truth Table:

| Input |   | Output |   |   |   |
|-------|---|--------|---|---|---|
| 0     | 0 | 1      | 0 | 0 | 0 |
| 0     | 1 | 0      | 1 | 0 | 0 |
| 1     | 0 | 0      | 0 | 1 | 0 |
| 1     | 1 | 0      | 0 | 0 | 1 |

**Output:**

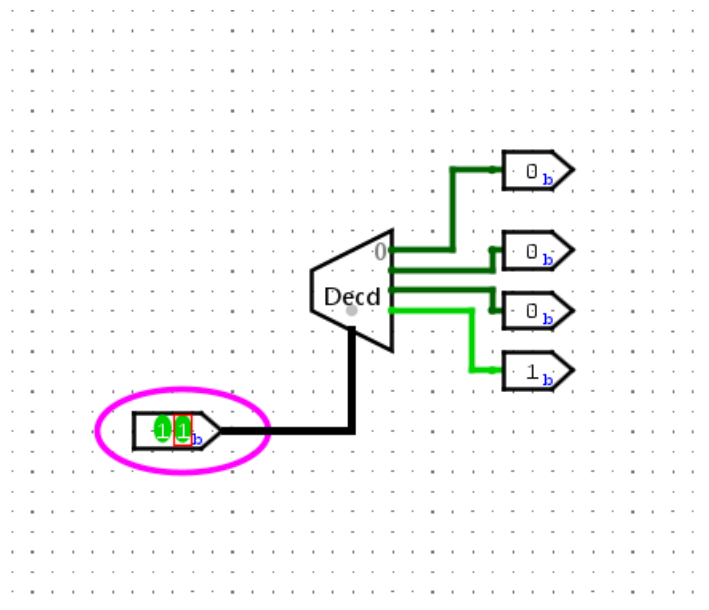

*“Heaven’s Light is Our Guide”*



## **Rajshahi University of Engineering & Technology**

### **Department of Computer Science & Engineering**

#### **Lab Report**

**Course Code: CSE 3108**

**Experiment No:2**

| <b>Submitted By:</b>   | <b>Submitted To:</b>   |
|--|--|
| <b>Name: Farzana Haider</b><br><b>Roll: 2003026</b><br><b>Section: A</b><br><b>Year: 3rd year Odd Semester</b> | <b>Name: Utsha Das</b><br><b>Lecturer</b><br><b>Department of CSE</b><br><b>RUET</b> |

**Name of the experiment:** Simulation of 4-bit Full Adder circuit using Logisim Evolution software.

**Theory:**

A full adder is a digital circuit that performs addition of three input bits: A, B, and a carry input (Cin). It produces a sum output (S) and a carry output (Cout). In this experiment, we aim to design a 4-bit full adder.

**Experiment:**

Table:

| A3  | A2  | A1  | A0  | B3  | B2  | B1  | B0  | Cin | Sum3 | Sum2 | Sum1 | Sum0 | Cout |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|------|------|------|------|------|
| 0   | 0   | 0   | 0   | 0   | 0   | 0   | 0   | 0   | 0    | 0    | 0    | 0    | 0    |
| 0   | 0   | 0   | 0   | 0   | 0   | 0   | 1   | 0   | 0    | 0    | 0    | 1    | 0    |
| 0   | 0   | 0   | 0   | 0   | 0   | 1   | 0   | 0   | 0    | 0    | 1    | 0    | 0    |
| 0   | 0   | 0   | 0   | 0   | 0   | 1   | 1   | 0   | 0    | 0    | 1    | 1    | 0    |
| 0   | 0   | 0   | 0   | 0   | 1   | 0   | 0   | 0   | 0    | 1    | 0    | 0    | 0    |
| 0   | 0   | 0   | 0   | 0   | 1   | 0   | 1   | 0   | 0    | 1    | 0    | 1    | 0    |
| 0   | 0   | 0   | 0   | 0   | 1   | 1   | 0   | 0   | 0    | 1    | 1    | 0    | 0    |
| 0   | 0   | 0   | 0   | 0   | 1   | 1   | 1   | 0   | 0    | 1    | 1    | 1    | 0    |
| ... | ... | ... | ... | ... | ... | ... | ... | ... | ...  | ...  | ...  | ...  | ...  |

**Output:**

